

Techniques for the global stability analysis of microwave circuits.

Application to novel circuit design.

Almudena Suárez

Dpto. Ingeniería de Comunicaciones
Universidad de Cantabria

OUTLINE

1 - Introduction

2 - Nonlinear dynamics of analog circuits

- Geometrical approach: the phase space
- Local stability
- Global stability. Bifurcations

3 - Simulation techniques

- Comparison
- Stability analysis
- Bifurcation analysis. Use of auxiliary generators

4 - Novel circuit design

5 - Conclusions

1 - INTRODUCTION

Nonlinear circuits: nonlinear differential equations

Steady-state solution:

- It can include autonomous and subharmonic frequencies
- DC, periodic, quasi-periodic, chaotic



Coexistence of solutions:

Same or different type

Stable (or physical) and unstable

When using frequency-domain analysis (intrinsically forced):

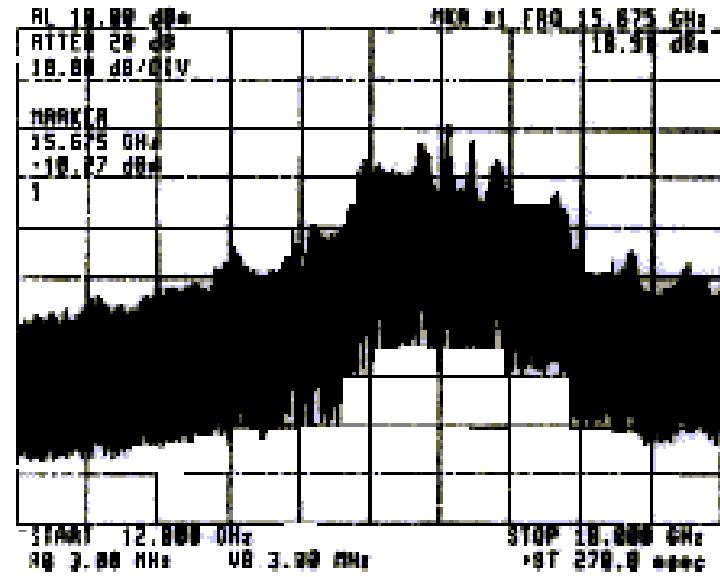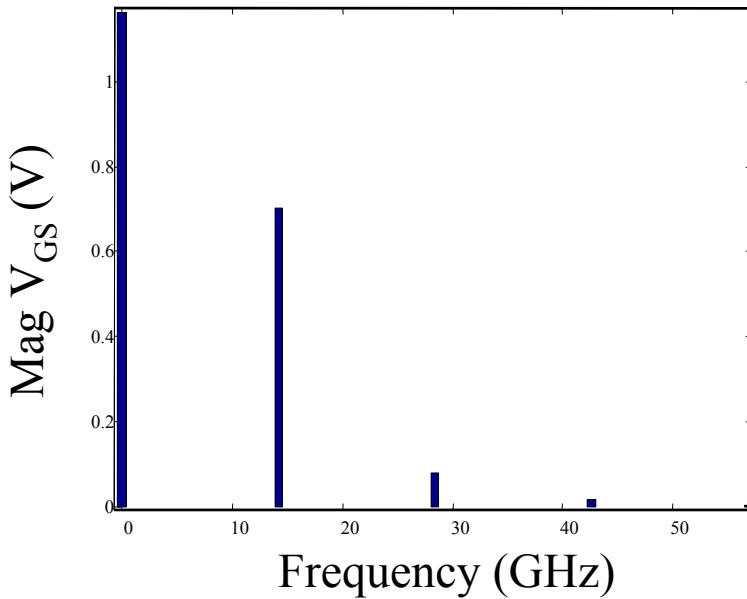Measured solution may be very different from the simulated one



Objective:

- Techniques for the global stability analysis of nonlinear circuits
 - Stability analysis under the variation of the circuit parameters


Applications:

- Accurate determination of stable-operation borders
- Investigation of complex behavior
- Advanced and novel circuit design. Practical examples

2 - NONLINEAR DYNAMICS OF ANALOG CIRCUITS



2.1- GEOMETRICAL APPROACH: THE PHASE SPACE

Current (A)

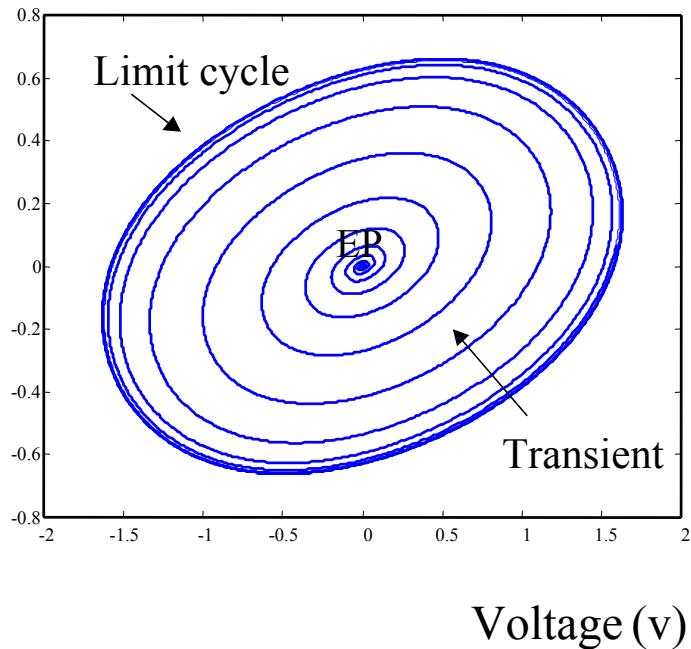

DC solution EP




Periodic solution LC

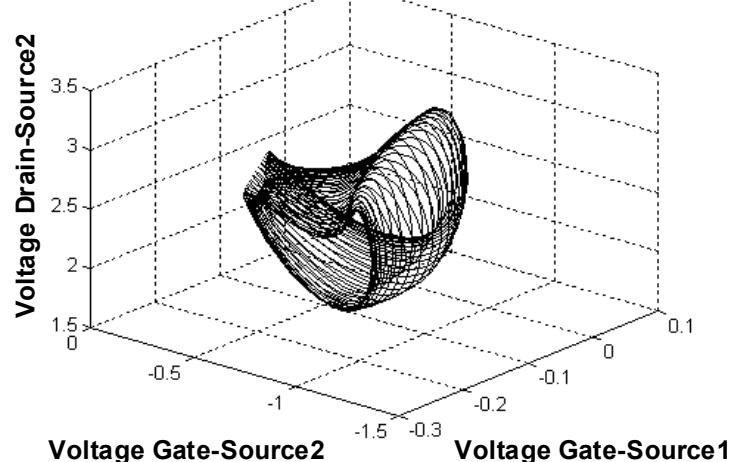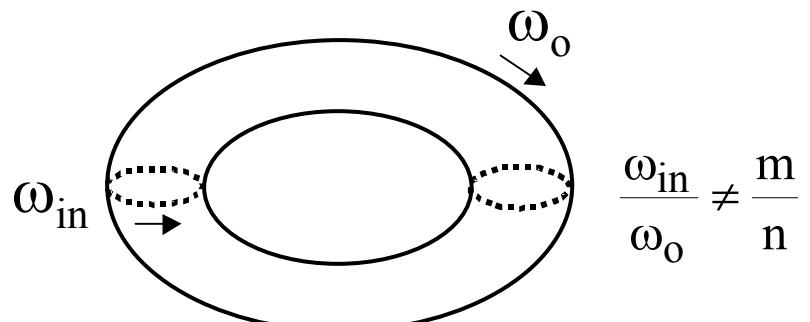

Quasi-periodic solution: Limit torus


Chaotic solution

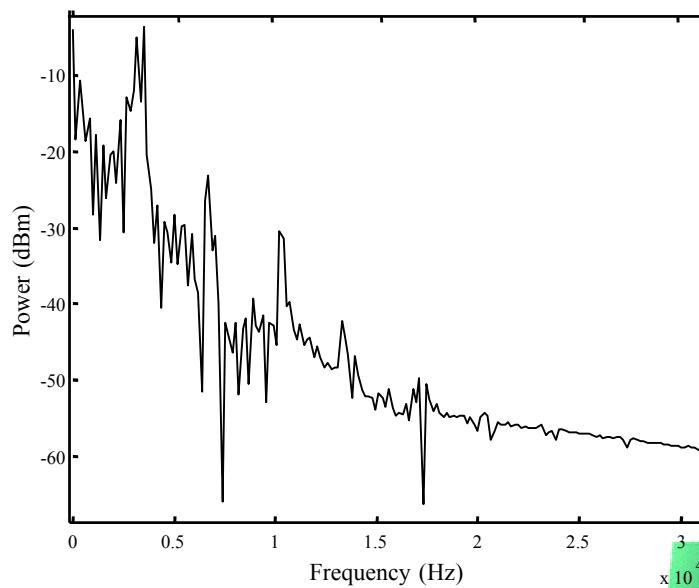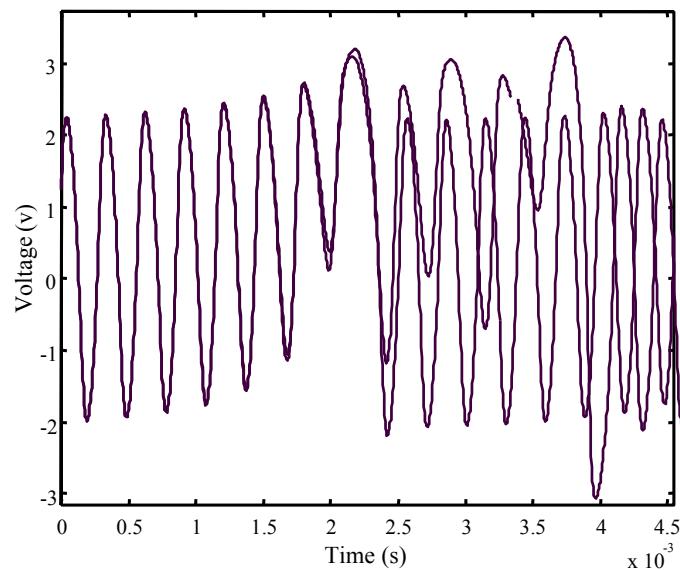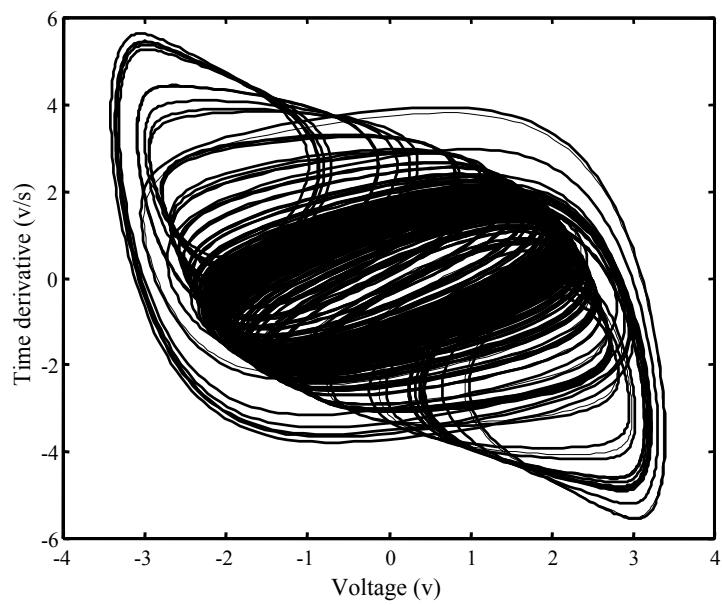- Sensitivity to initial conditions
- Continuous spectrum
- Fractal dimension




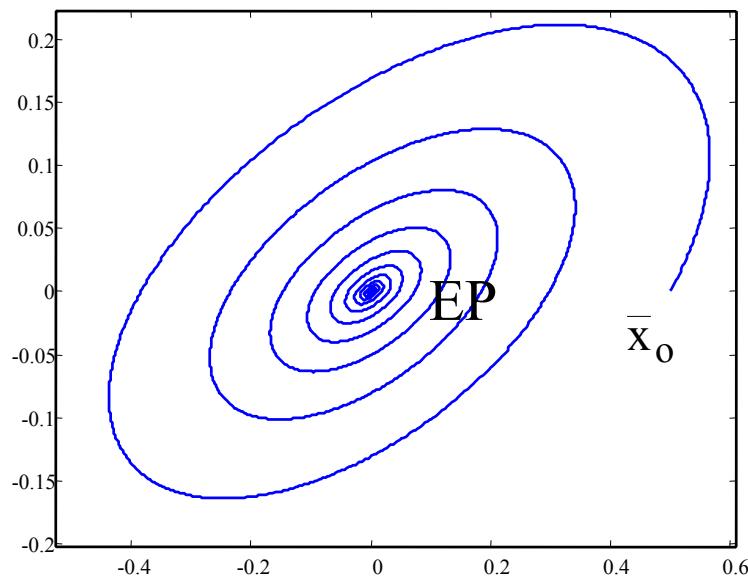2.2 - LOCAL STABILITY OF STEADY-STATE SOLUTIONS

Through small amplitude perturbations: $\bar{\varepsilon}(t)$



Stable EP

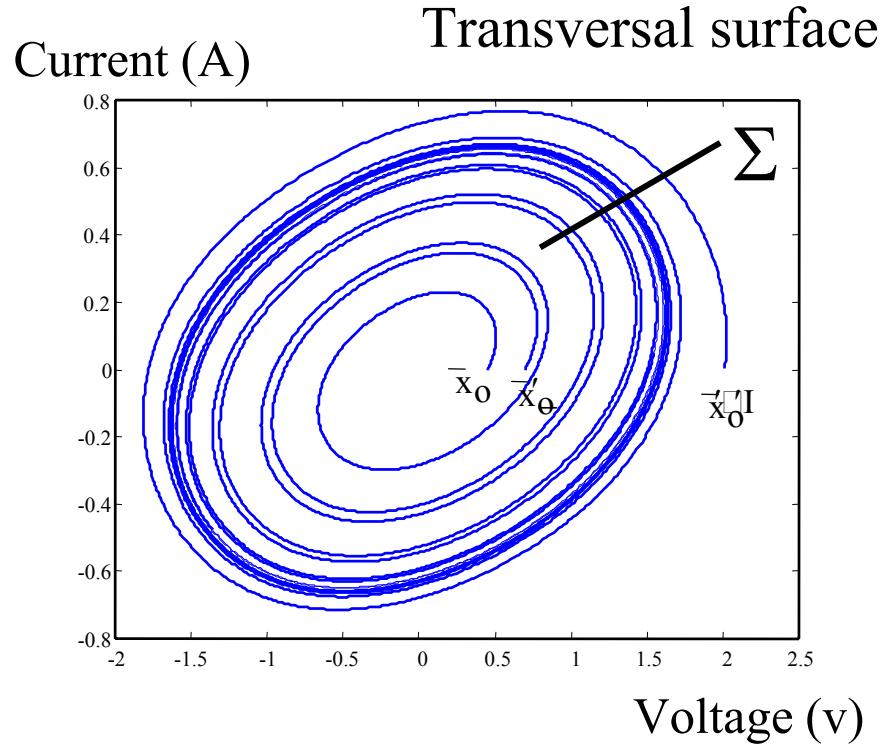




Stable LC

Stability types:


Equilibrium point or

intersection point with a transversal surface Σ

(limit cycle in phase space)

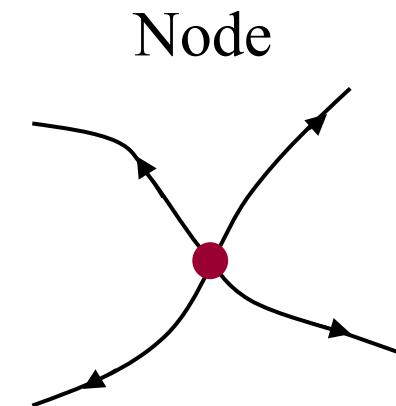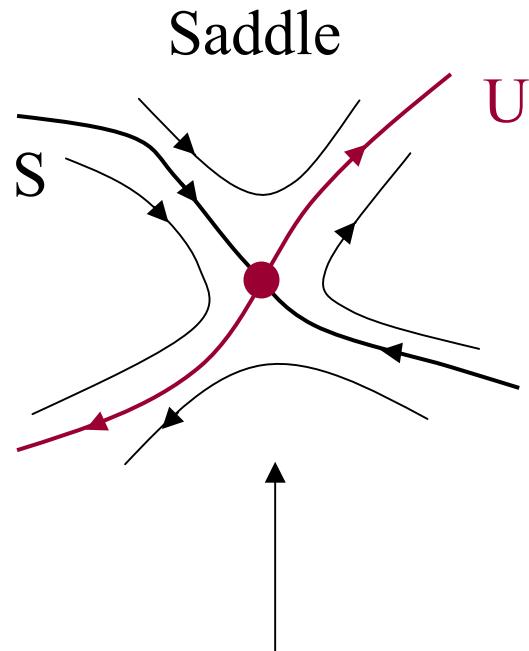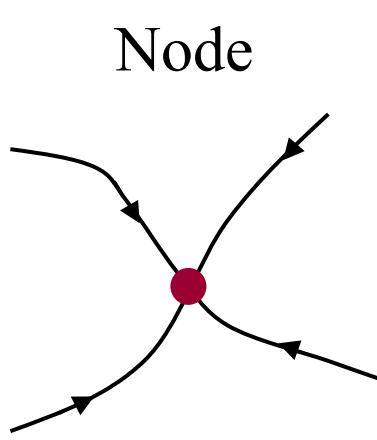

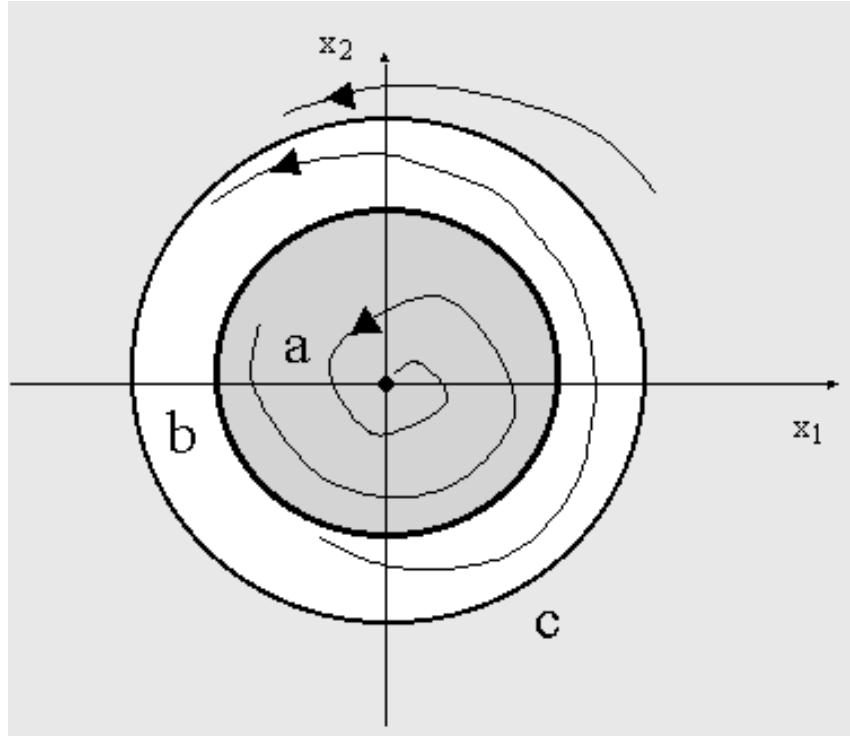Coexistence of stable and unstable steady-state solutions :



Stable and unstable solutions alternate

Different **basins of attraction**

2.3 - GLOBAL STABILITY

Variations in one or more circuit parameters η :


Input generator
linear element value

Bifurcation

- *Qualitative* variation of the solution **stability** under *continuous* modification of η
- *Creation / destruction* of solutions

Example Onset of a free-running oscillation

EP \longrightarrow Limit cycle

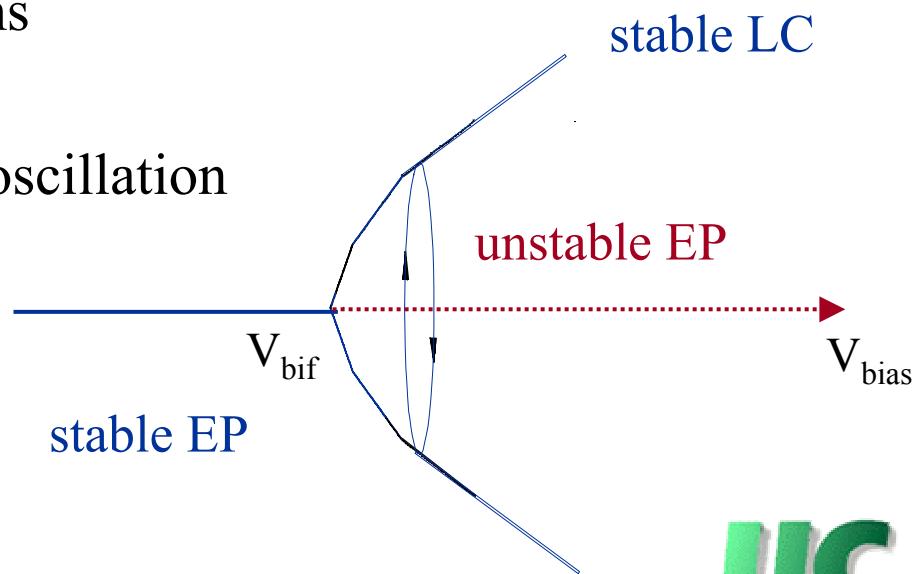


3 - SIMULATION TECHNIQUES

3.1 - COMPARISON

- Time-domain integration

Natural circuit evolution (Physical)

All types of steady-state solutions

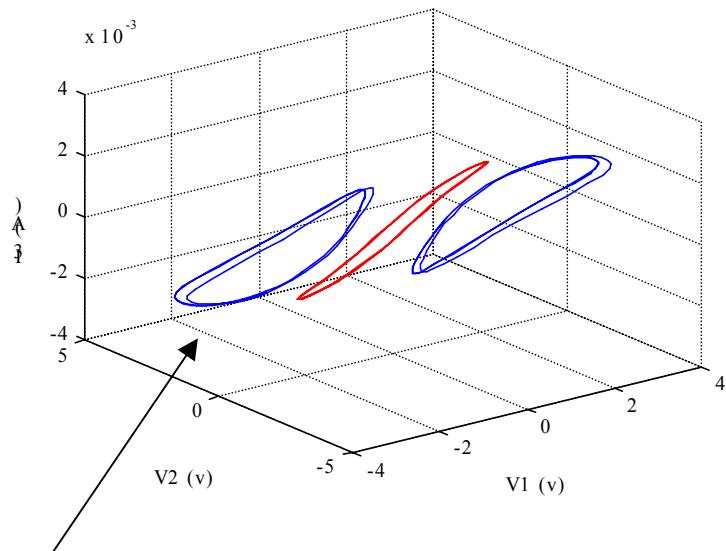

Small basin of attraction

- Harmonic balance

Transient is avoided
Continuation techniques

Drawbacks:


Difficulty in autonomous and subharmonic regimes

Convergence to unstable solutions
(stability analysis required)

Limited to periodic and quasi-periodic solutions

3.2 - STABILITY ANALYSIS

External Generator

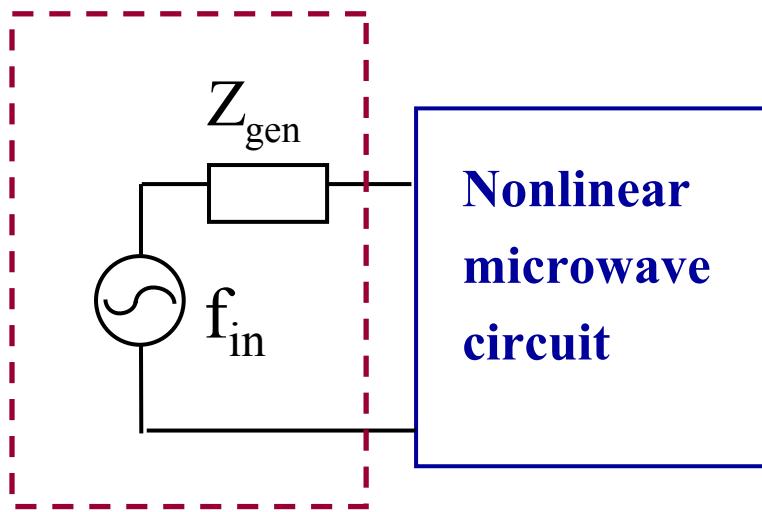

$$\bar{H}(\bar{X}) = 0$$

$$x_p(t) = \sum_m X_m e^{j(m\omega_{in})t}$$

- **Perturbation:** $e^{(\sigma + j\omega t)}$
- **Linearization:** $[JH(K\omega_{in} + \omega - j\sigma)] \bar{\Delta X} = 0$
- **Determinant:** $\det[JH(K\omega_{in} + \omega - j\sigma)] = 0$

3.3 - BIFURCATION ANALYSIS

Local bifurcation conditions


$$\det [JH (jk\omega_{in} + j\omega_b)] = 0$$

$$\left. \frac{d\sigma}{d\eta} \right|_{\eta=\eta_b} \neq 0$$

$\omega_b \neq \frac{m}{n} \omega_{in}$ Hopf

$\omega_b = \frac{\omega_{in}}{2}$ I or Flip

$\omega_b = 0$ Turning point / Pitchfork

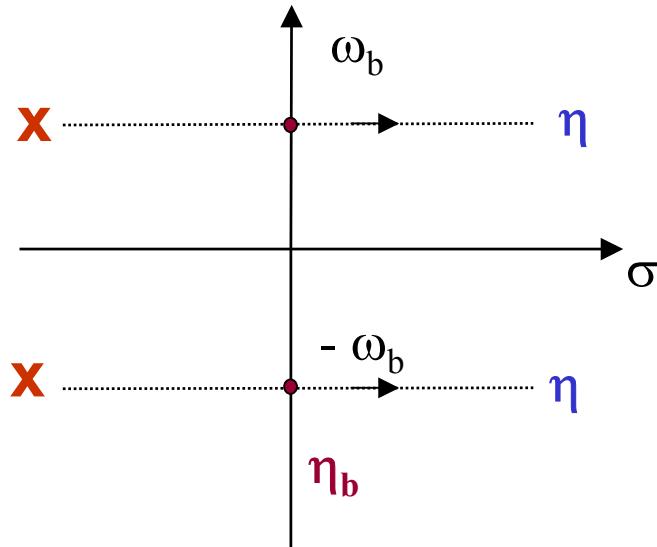

→ Det complex, η_b, ω_b

→ Det real, η_b



→ Det real, η_b

Bifurcation diagrams

- Turning points $\omega_b = 0$

Jump and hysteresis


- Branching - type bifurcations

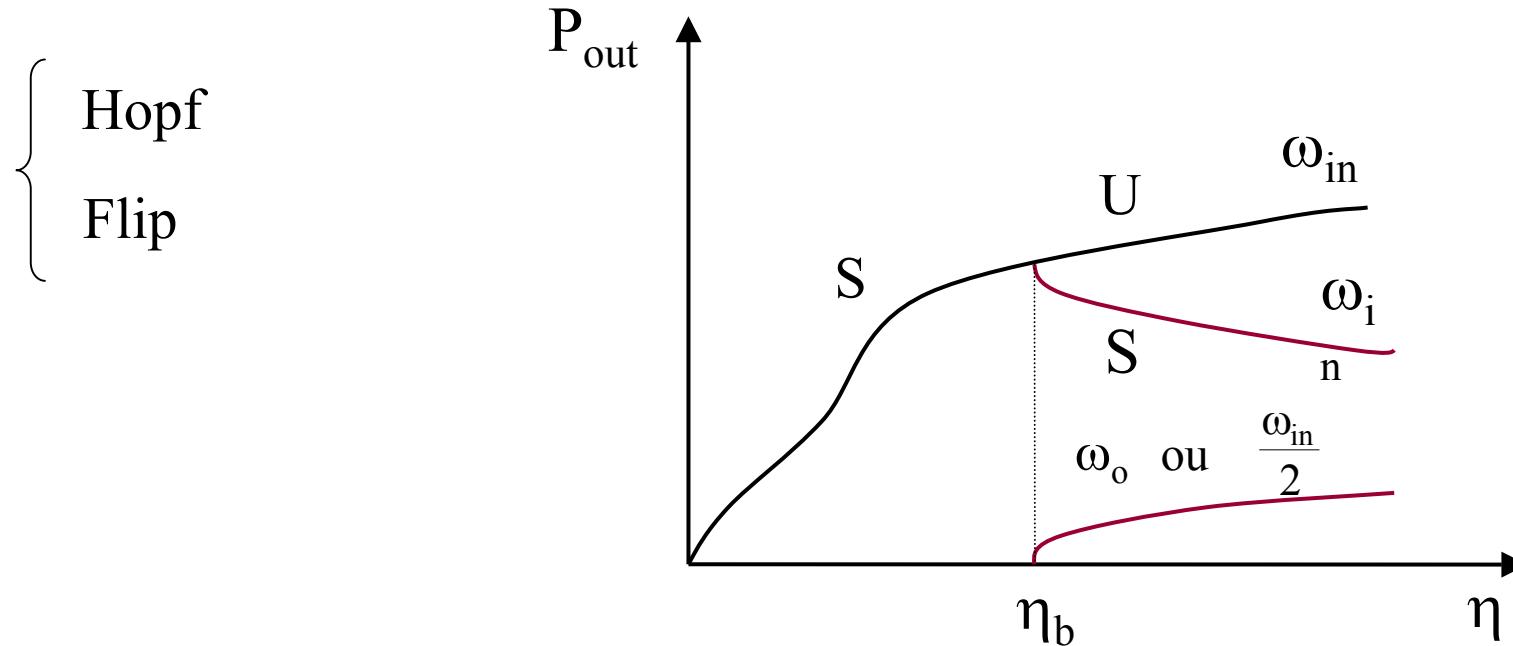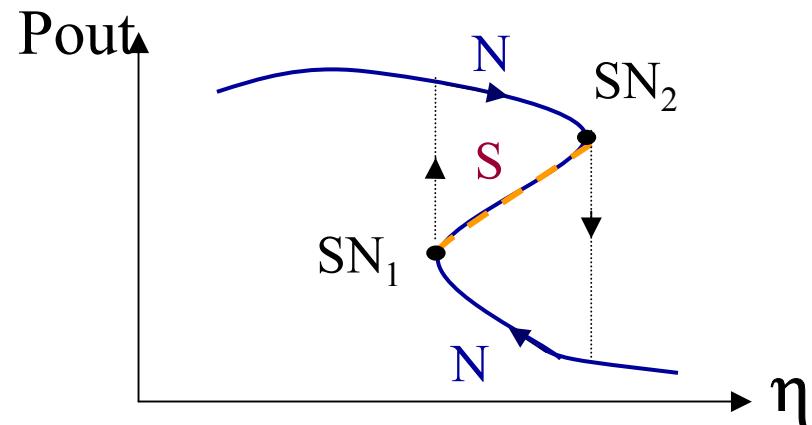


Global bifurcations

- Saddle connection
- Mode-locking at saddle-node : Synchronization / synchronization loss

Bifurcation diagram

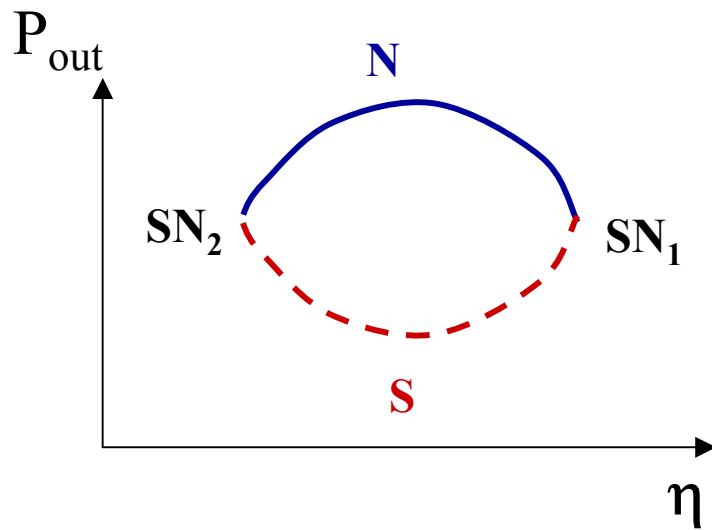


Poincaré map

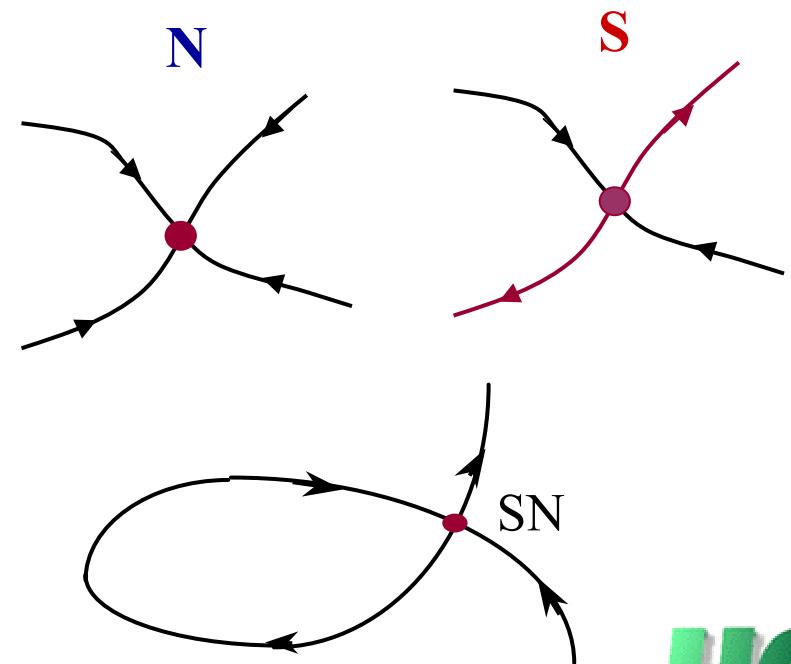

Autonomous and subharmonic solutions:
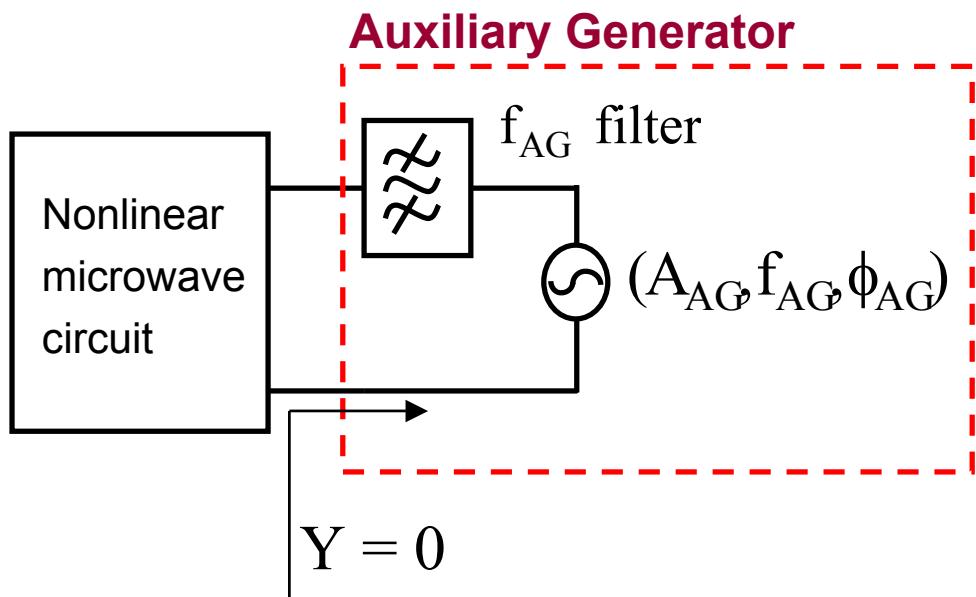
$$\bar{X}^0 = [A_g] \bar{G} \longrightarrow \text{Leads to trivial mathematical solutions}$$



- 2 more unknowns:


$$\begin{cases} A_{AG}, f_{AG} & \text{Autonomous} \\ A_{AG}, \phi_{AG} & \text{Synchronized} \end{cases}$$

- 2 more equations:

$$\begin{cases} Y_r = 0 \\ Y_i = 0 \end{cases}$$


- Stability analysis of steady-state regimes

External Generator

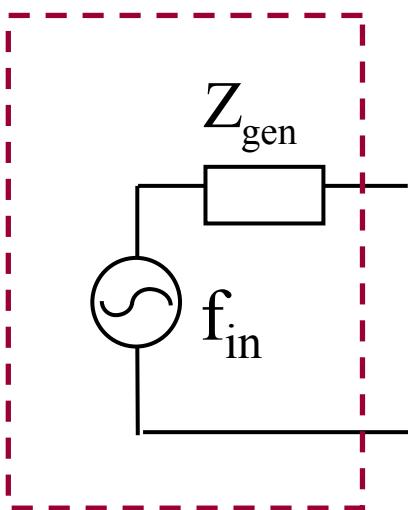

**Nonlinear
microwave
circuit**

Auxiliary Generator

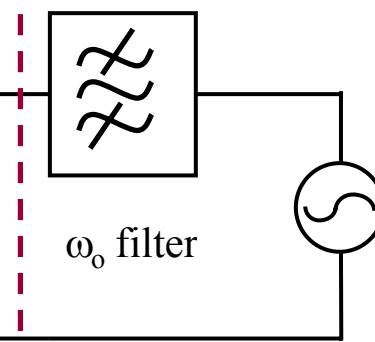

(ε, ω_0)


$Y(\omega_0)$

$$\operatorname{Re} Y(\omega_0) < 0$$

$$\operatorname{Im} Y(\omega_0) = 0$$

Combined with zero-pole identification techniques


- Continuation techniques

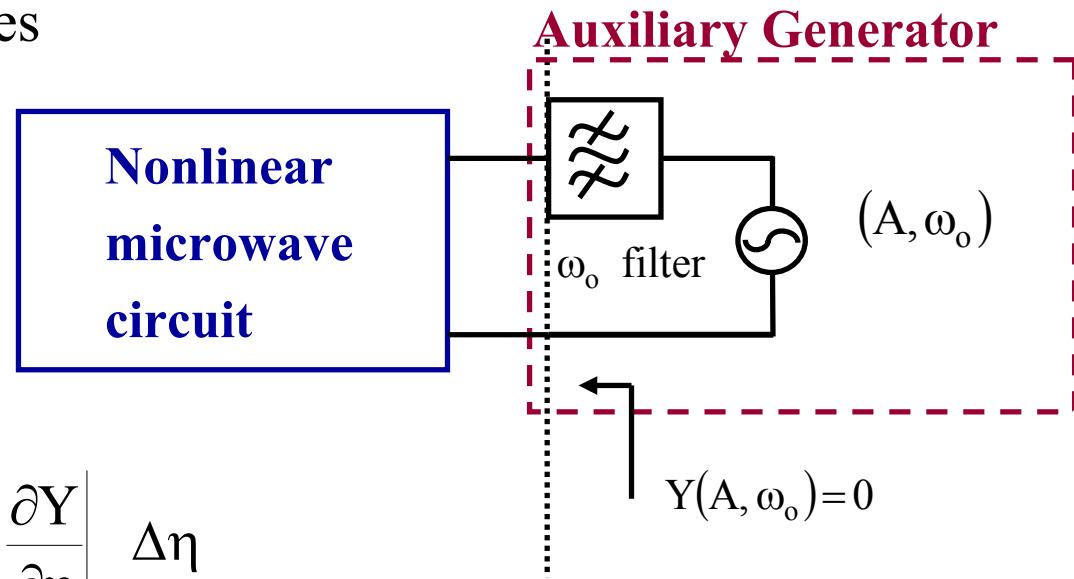

$$\begin{bmatrix} A^{n+1} \\ \omega_0^{n+1} \end{bmatrix} = \begin{bmatrix} A^n \\ \omega_0^n \end{bmatrix} - [JY]_n^{-1} \left. \frac{\partial Y}{\partial \eta} \right|_n \Delta \eta$$

AG jacobian matrix:
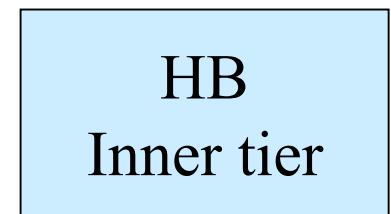
$$[JY] = \begin{bmatrix} \frac{\partial Y_r}{\partial A} & \frac{\partial Y_r}{\partial \omega_0} \\ \frac{\partial Y_i}{\partial A} & \frac{\partial Y_i}{\partial \omega_0} \end{bmatrix}$$






Comparison of increments $\{\Delta\eta, \Delta A, \Delta \omega_0\} \rightarrow$ Parameter switching

Continuation technique

Application to VCO

$Y = 0$ Optimization goal

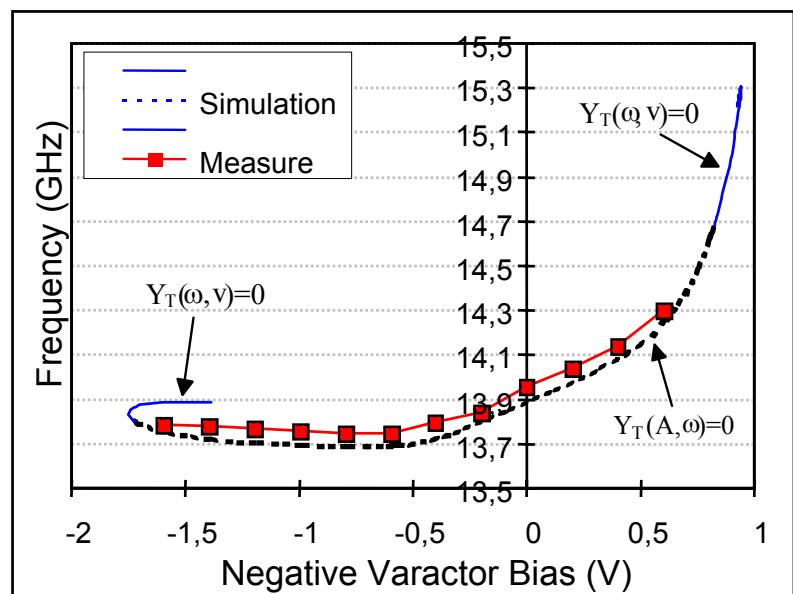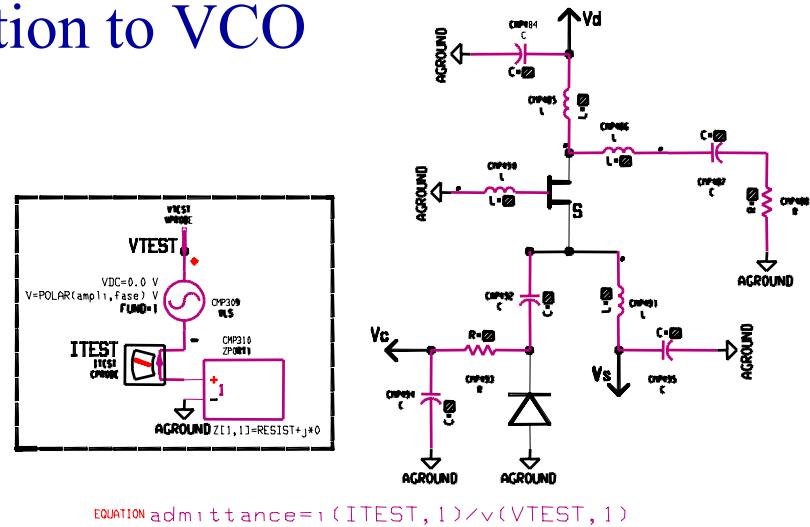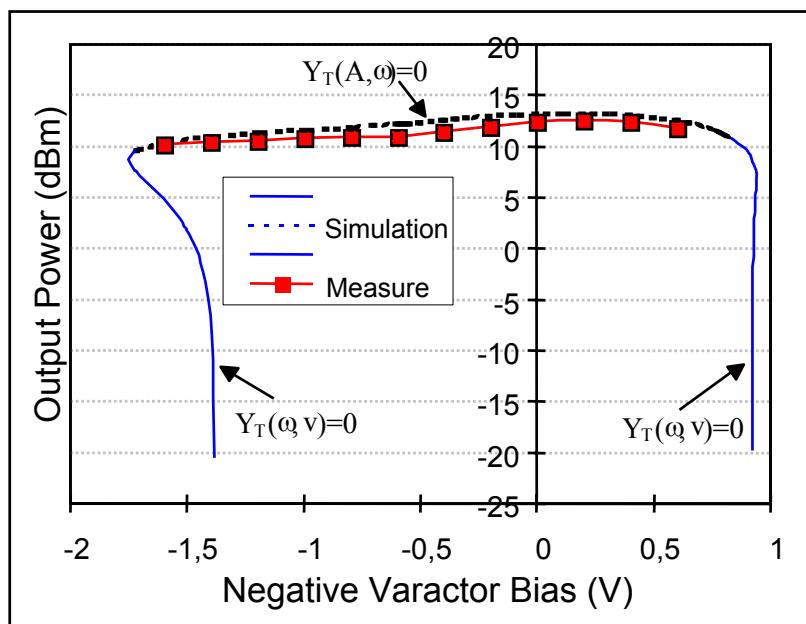

- Simple bifurcation conditions

AG jacobian matrix:


$$[JY] = \begin{bmatrix} \frac{\partial Y_r}{\partial A} & \frac{\partial Y_r}{\partial \omega_o} \\ \frac{\partial Y_i}{\partial A} & \frac{\partial Y_i}{\partial \omega_o} \end{bmatrix}$$


$$\begin{bmatrix} A^{n+1} \\ \omega_o^{n+1} \end{bmatrix} = \begin{bmatrix} A^n \\ \omega_o^n \end{bmatrix} - [JY]_n^{-1} \left. \frac{\partial Y}{\partial \eta} \right|_n \Delta \eta$$

Saddle-node bifurcation locus

$$\begin{cases} \det(A, \omega_o, \eta_1, \eta_2) = 0 \\ Y_r(A, \omega_o, \eta_1, \eta_2) = 0 \\ Y_i(A, \omega_o, \eta_1, \eta_2) = 0 \end{cases}$$

$$\det [JY] = 0$$

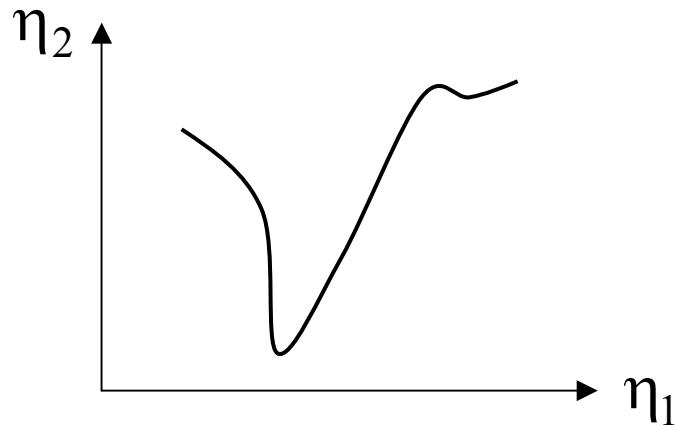

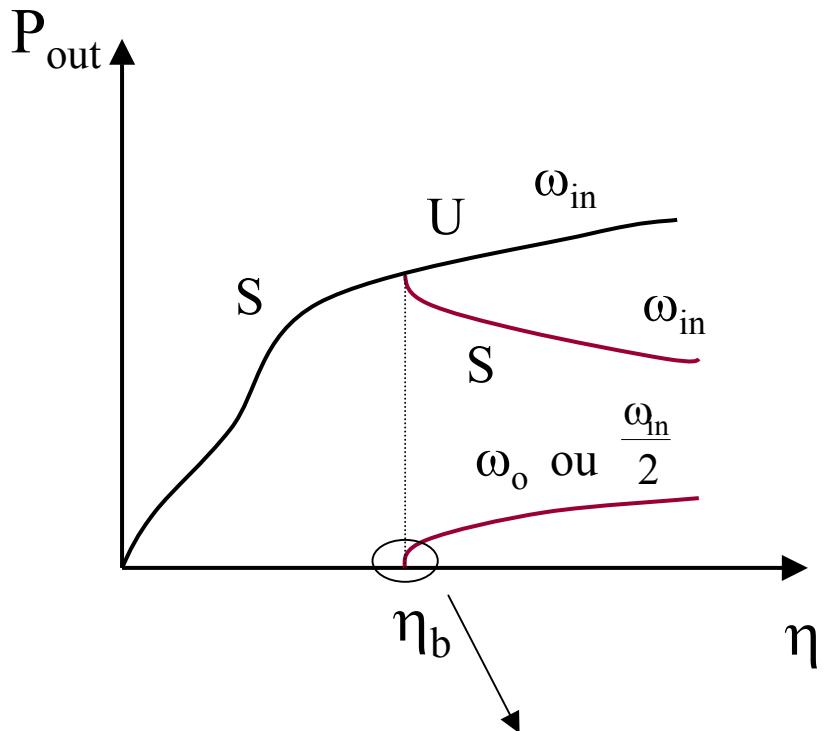

New branch starts at zero amplitude

Hopf-type bifurcation locus

$$A = \varepsilon, \quad \phi = 0$$

$$\begin{cases} Y_r(\omega_0, \eta_1, \eta_2) = 0 \\ Y_i(\omega_0, \eta_1, \eta_2) = 0 \end{cases}$$


Flip-type bifurcation locus


$$A = \varepsilon, \quad \omega_0 = \frac{\omega_g}{2}$$

$$\begin{cases} Y_r(\phi, \eta_1, \eta_2) = 0 \\ Y_i(\phi, \eta_1, \eta_2) = 0 \end{cases}$$

Bifurcation loci

Frequency divider 28-14 GHz

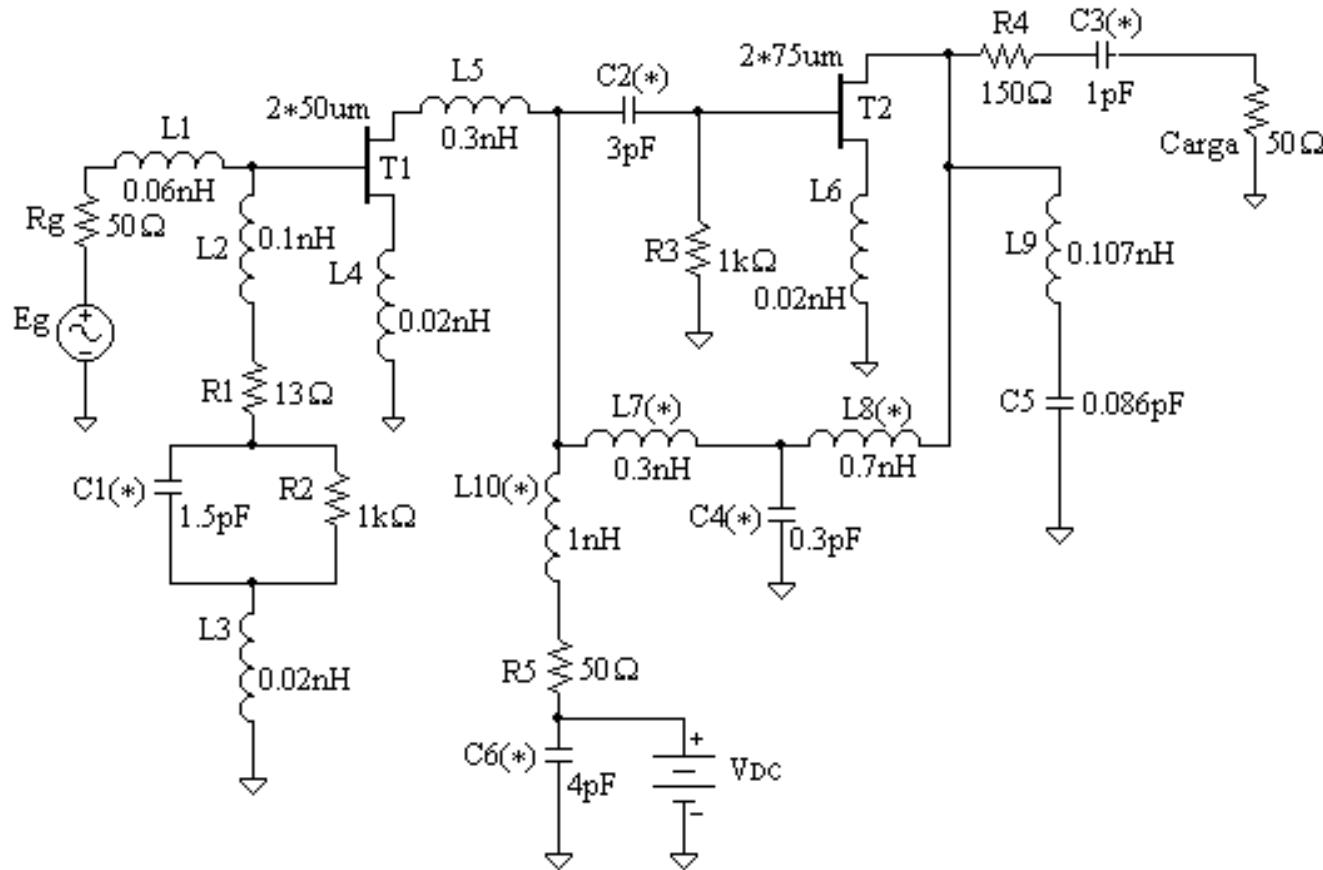


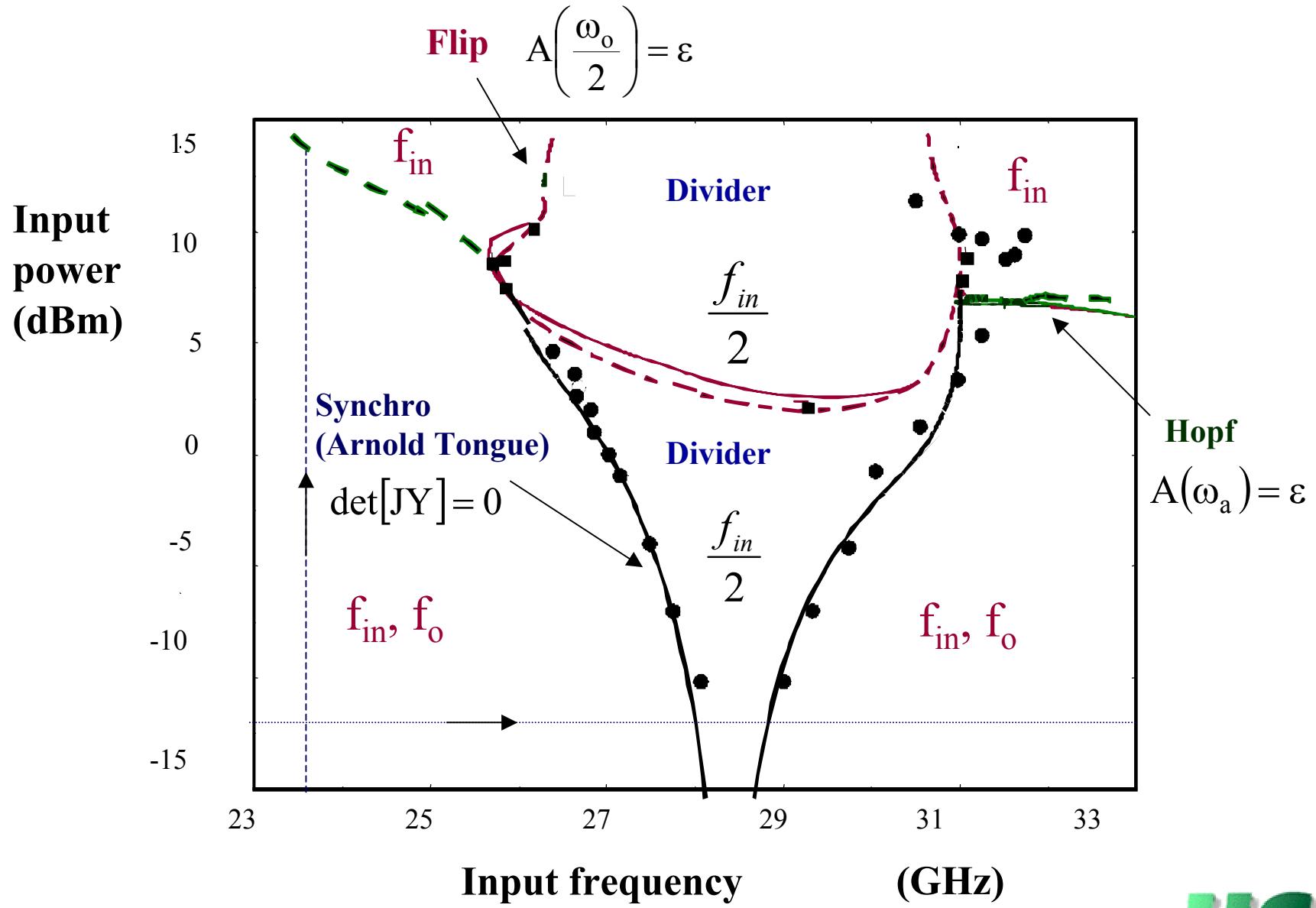

Bifurcation diagram


S : Synchronization

T : Turning point (jump)

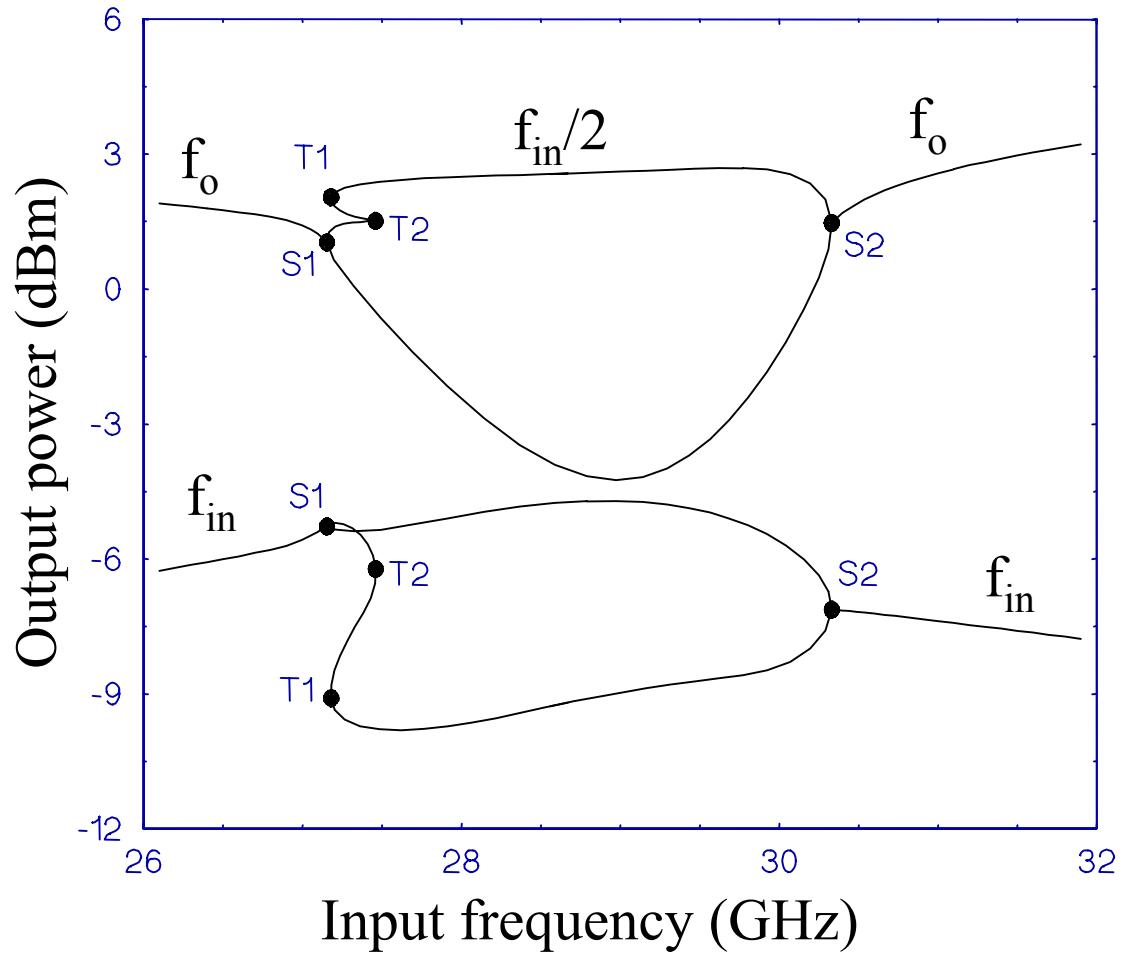

4 - NOVEL CIRCUIT DESIGN



4.1 - SELF-OSCILLATING MIXERS

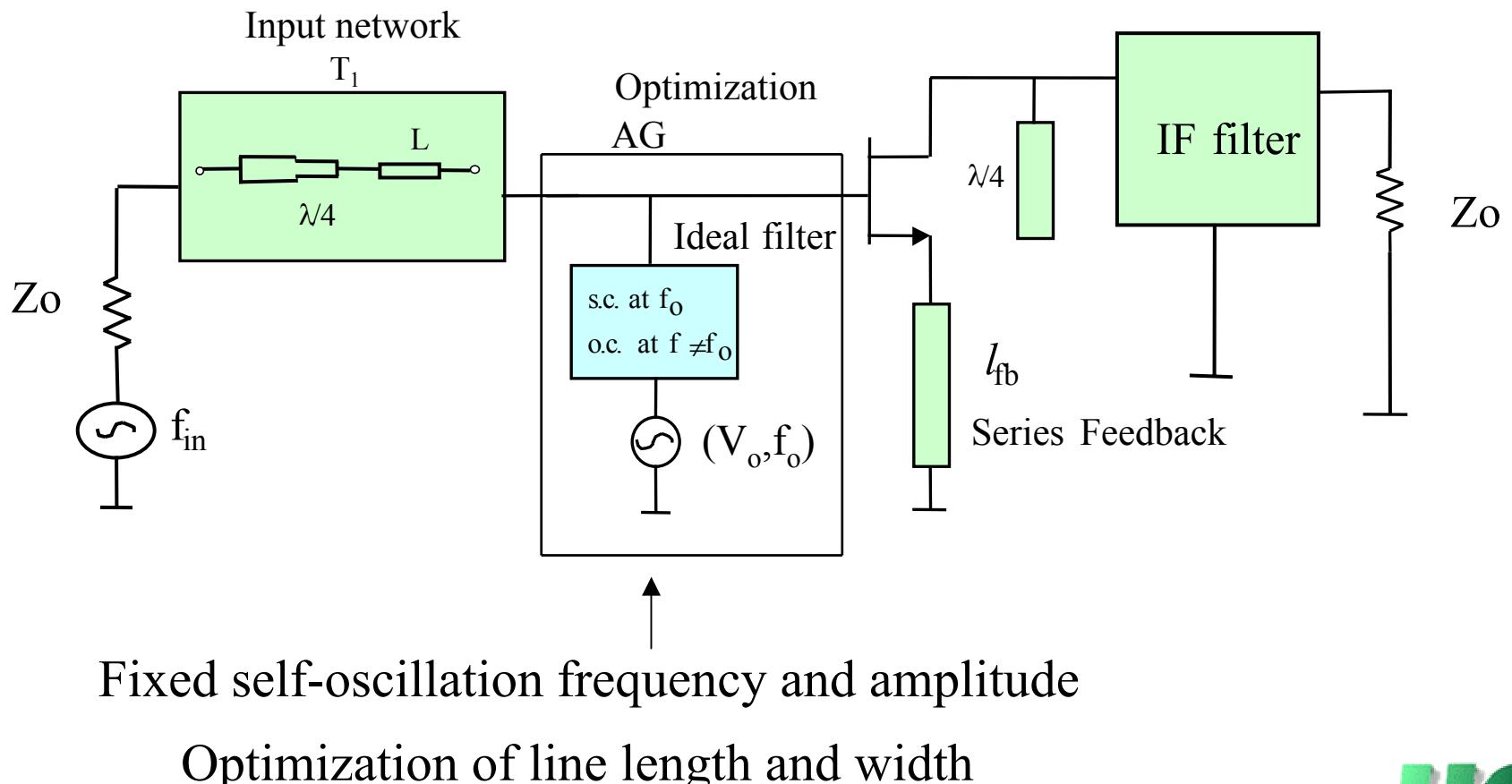

Shift of inverse-Hopf bifurcation

$Y_T(\gamma_1, \gamma_2) = 0$ with $V_o = 10^{-2}$ V, $f_o = 5$ GHz, $P_{in} = P_{inH}^k$ (Inverse Hopf)

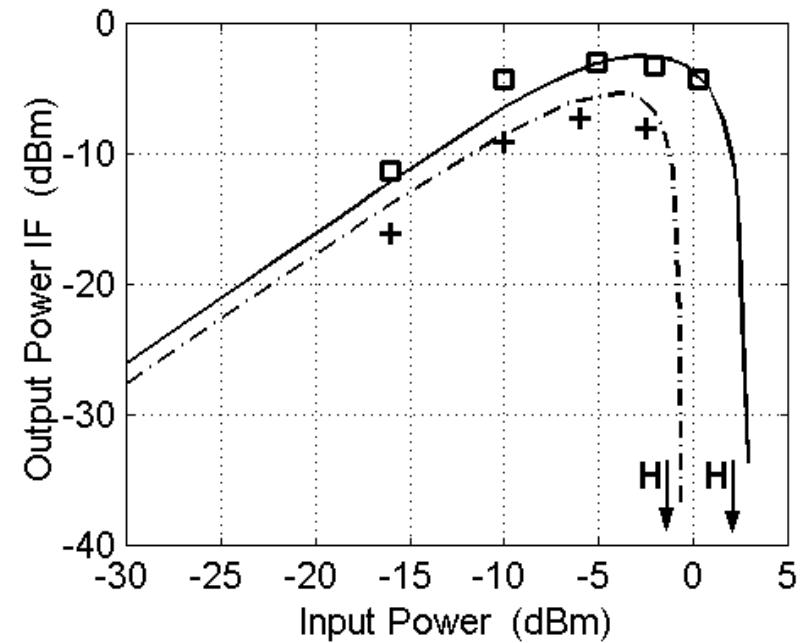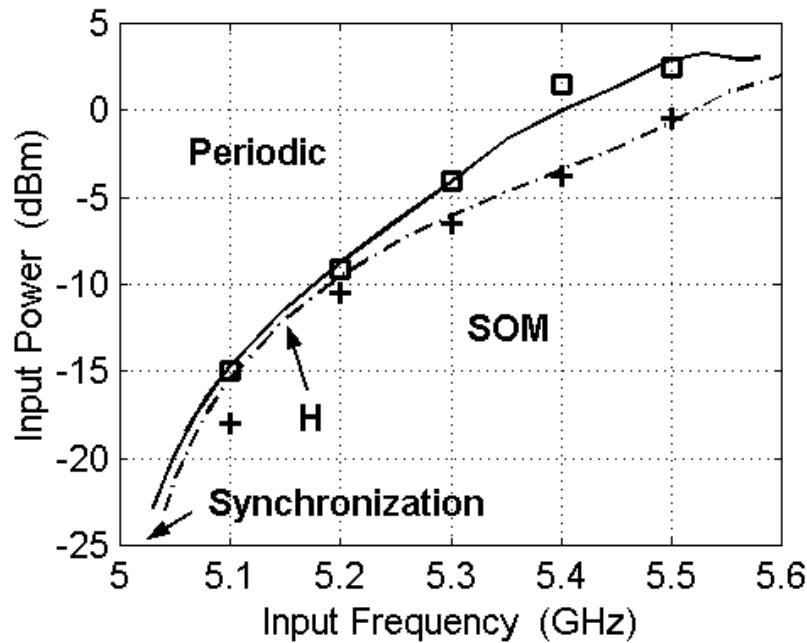$Y_T(\gamma_1', \gamma_2') = 0$ with $V_o = 0.8$ V, $f_o = 5$ GHz, $P_{in} = 0$ W (Free-running oscillator)





4.2 - ANALOG FREQUENCY DIVIDER BY VARIABLE ORDER 6 TO 9

Arnold tongues of very nonlinear oscillators

Period-adding routes to chaos

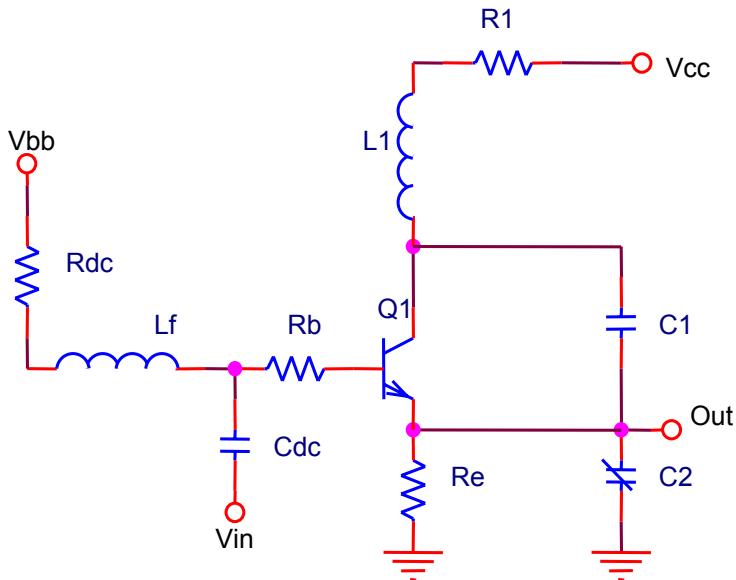
Colpitts-type oscillator in very nonlinear regime



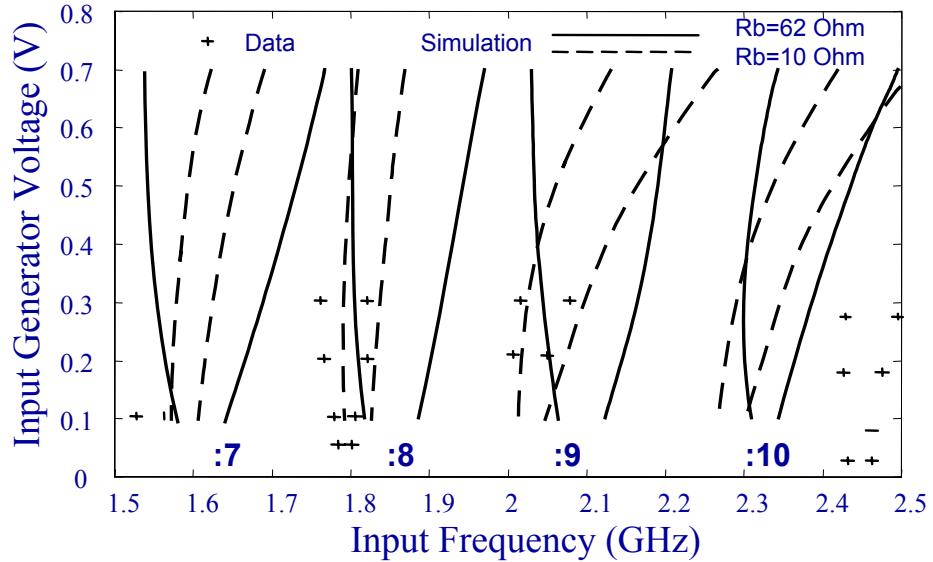


Arnold tongues


Period-adding
sequence

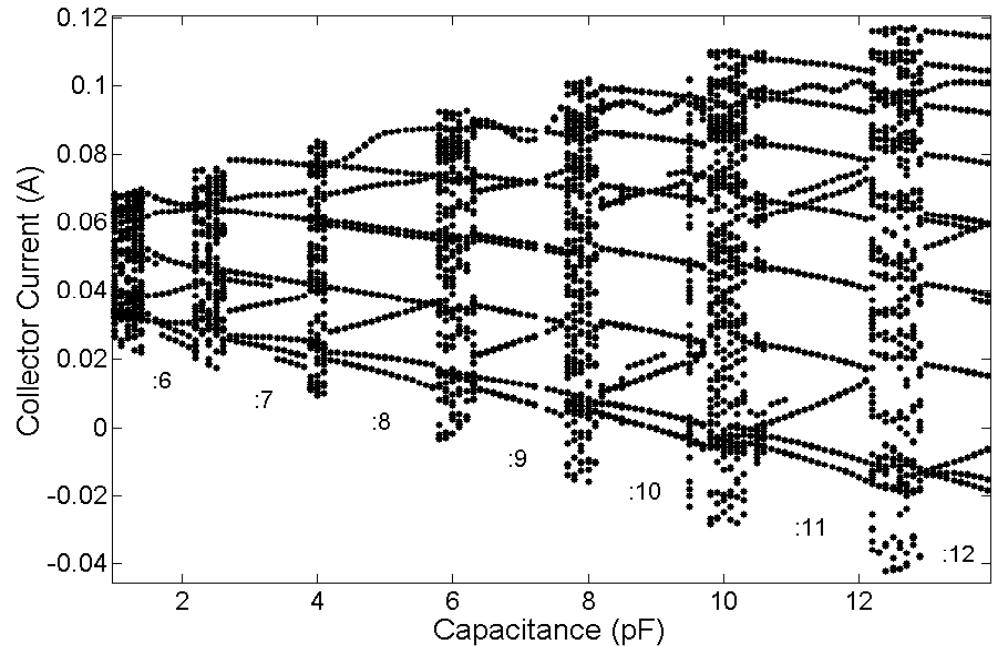


Experimental results

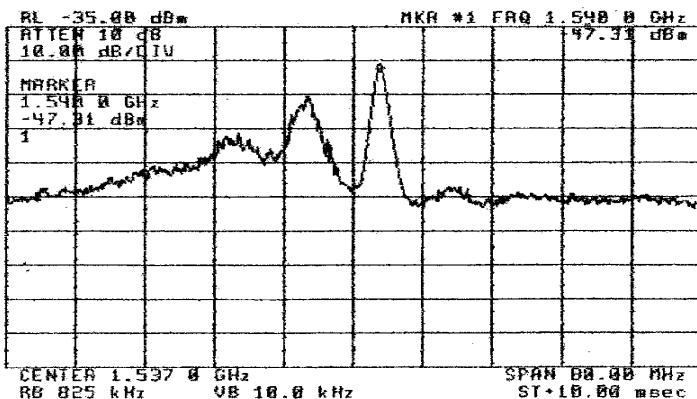

Near-synchronization spectrum

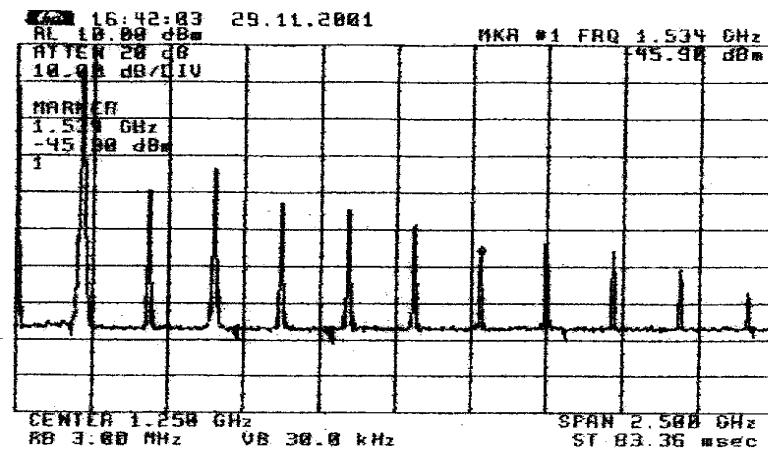

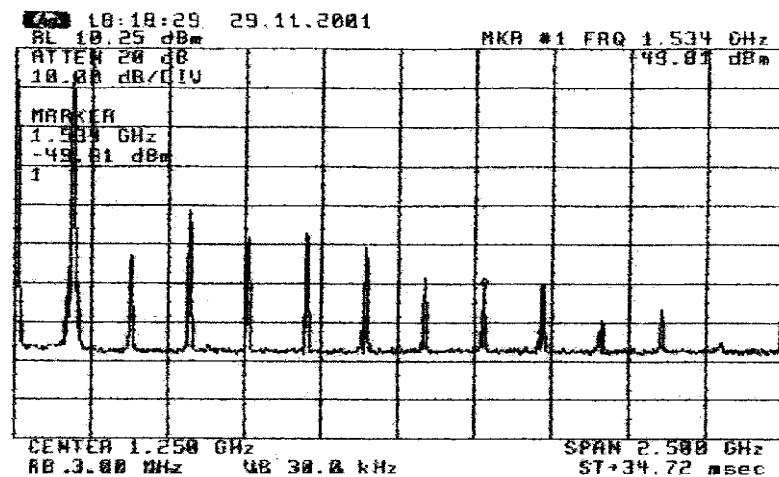Division by 7, $f_{in} = 1.534 \text{ GHz}$ ($C_1 = 2.9 \text{ pF}$)



Division by 8, $f_{in} = 1.534 \text{ GHz}$ ($C_1 = 4.7 \text{ pF}$)

Conclusions

Nonlinear microwave circuits → Coexistence of solutions
Bifurcations

Bifurcations delimit operation borders. They precede chaotic behavior

Continuation techniques → Easily combined with harmonic balance

Difficulty with autonomous and synchronized regimes:
solved through auxiliary generators

Auxiliary generators enable simple techniques for bifurcation detection

Novel circuit design:

- Fixing of oscillation point
- Fixing of bifurcation point (SOM)
- Use of Arnold tongues and period-adding routes to chaos

Variable-order frequency dividers